

Inverting Buck Regulator Saves Space and Power

Designers are periodically faced with the requirement to generate a negative voltage rail in order to provide a bias voltage for applications using sensors which read signals both above and below ground. For many engineers, the first thought will be to use inverting regulated charge pumps: in fact, these are ideal for handheld applications where the output voltage required is less than -5V and the input is typically a lithium-ion battery. In applications that require negative voltages greater than -5V, SEPIC inverters and transformer-based designs can also produce a positive-to-negative voltage conversion, but only at the cost of complexity and a high component count. Now the AS7620 IC helps designers to solve these problems.

Mark Shepherd, Field Applications Engineer, Austriamicrosystems, Unterpremstätten, Austria

Inductor-based switching buck inverters offer the benefits of good efficiency with low component count. Depending on the buck inverter, they can provide high efficiencies over both a wide dynamic load and input range, an area where charge pumps tend to fall down due to their seesaw efficiency curves. The designer must be mindful of the total system power consumption in a scenario in which a -5 V rail must be generated from a 12 V or 24 V system voltage. For instance, a sensor application might require a -5 V bias voltage at a 1-200 mA load range, operating from a 24 V system supply feeding multiple sensors distributed through a building. The designer could connect an inverting charge pump to the 5 V output that has been stepped down from the 24 V system rail to provide the -5 V. The efficiency of such a circuit, however, would be the product of the charge pump's efficiency - typically 70 % - and the efficiency of the step-down regulator - typically 90 %. This gives an overall system efficiency of 63 %. Multiplied across multiple sensors, this loss can add up.

This brings into focus the advantages of implementing an inverting buck regulator circuit, a simple technique that involves exchanging V_{out} with ground on a buck regulator. Not all buck regulators can be used this way, however, since the inversion of V_{out} with ground can introduce a right half plane (RHP) zero in its control-to-output transfer function, opening up the regulator to the risk of instability.

Figure 1 shows a -5V negative buck/boost inverter circuit, using the AS7620 positive buck regulator from austriamicrosystems. This IC is specified for a 3.6 V to 32 V input voltage range, uses a 1.2 V feedback voltage and has an internal 500 mA power switch. The switch current is monitored so that the converter always operates in discontinuous current mode (DCM): this means that it is intrinsically stable, and no external compensation circuitry is needed. It also means that it does not have an issue with stability due to the RHP zero, because this only occurs in flyback, boost and Ćuk circuits, and then only in continuous current mode.

As mentioned earlier, by exchanging V_{out} with ground, it is possible to invert the polarity and produce a negative output voltage. Since the circuit topology is now that of a buck/boost circuit, it might in theory seem attractive to use the part in both boost and buck mode. In practice, however, the efficiency of the buck/boost topology when in boost mode barely exceeds 60 %. In buck mode, efficiency is far higher (see Figure 2).

Careful specification of the inverting buck regulator pays dividends in light-load applications in particular. As Figure 2 shows, high efficiency is maintained all the way down to a 1 mA load current, and this is a consequence of the AS7620's low internal quiescent current (37 μ A).

Operation of the inverting buck/boost regulator

During the first stage of the switching period, when the switch is on, the inductor is linearly ramped up to store energy (see Figure 1 again). No current passes to the output. In the second stage,

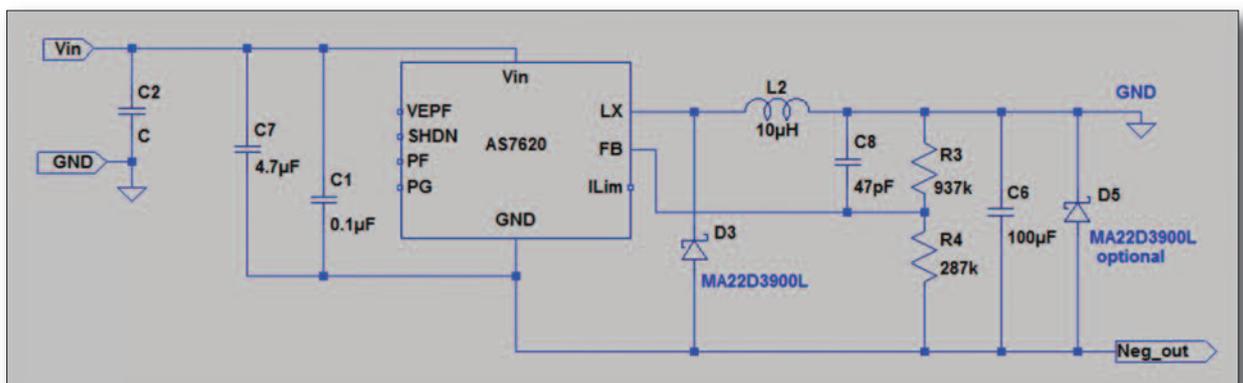


Figure 1: AS7620 connected as a negative buck/boost regulator

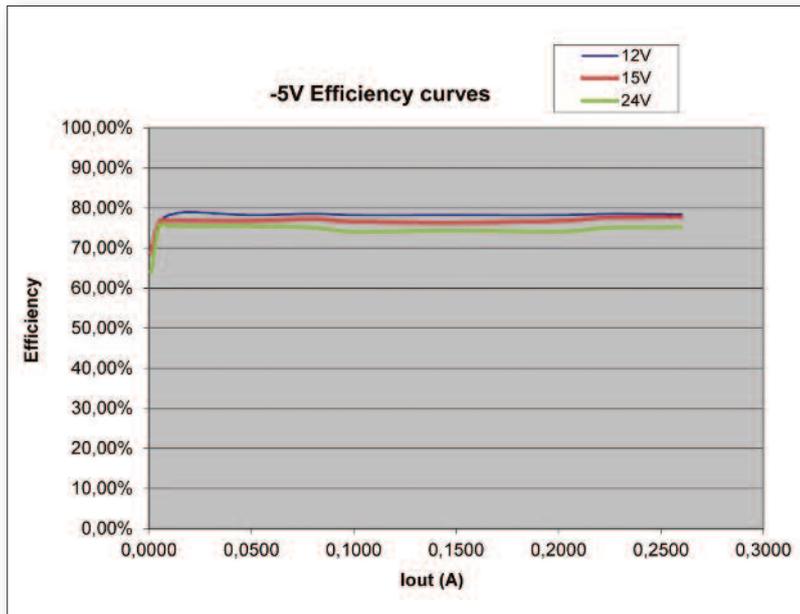


Figure 2: Efficiency curves of AS7620 in buck mode supplying a -5V output

when the internal switch in the IC turns off, the inductor will reverse polarity, inducing the freewheeling diode D3 to forward-bias and transfer energy to the load and the output capacitor C6. The only energy to reach the output via the diode is the energy stored in the inductor - none comes directly from the input DC source. The output voltage is negative because the switch node is negative in reference to ground.

This circuit gives rise to a number of characteristics that are not obvious at first glance, and that must be taken into account if the design is to operate effectively.

1) The voltage across the AS7620 is made up not only of V_{in} , but is equal to the input voltage plus the magnitude of the negative output voltage ($V_{in} + |V_{out}|$). Therefore care should be taken to specify an appropriate voltage rating for the input caps (C7 and C1 in Figure 1). In addition, ($V_{in} + |V_{out}|$) must not exceed the maximum voltage rating of the regulator. The AS7620, for instance, has a maximum voltage rating of 40 V. It is feasible to use this part to generate a -12 V output from a +12 V rail, or a -5 V output from a +24 V rail.

- 2) The switch currents in the buck/boost configuration are necessarily higher than in the buck topology, thus lowering the available output current. The start-up input current of the buck/boost converter is also higher than in the standard buck-mode regulator, and this might overload an input power source that has a current limit set too low. For this reason, the buck/boost circuit employing the AS7620 has an efficiency sweet spot of 1-250 mA at input voltages of 12 V and higher. At voltages below 12 V, the negative output current capability of the part will need to be decreased to 170 mA at most.
- 3) The circuit's Shutdown pin is left floating. The AS7620 provides an internally regulated pull-up circuit, so the device can be shut down if the SHDN pin is pulled to the GND pin (which is the negative output voltage). Since the GND pin of the AS7620 is the negative output voltage in an inverting application, it will be necessary to use a level-shifting circuit, connected to an open drain, to shut the part down. If Shutdown is not used, the pin should be left floating, and no trace should be connected to it in order to minimise noise injection.
- 4) The current coming from the input capacitor will be choppy because of the switching operation of the internal FET, so care should be taken to provide enough input capacitance; 4.7-10 μ F is sufficient.

The output current will also be choppy because of the diode current transitions.

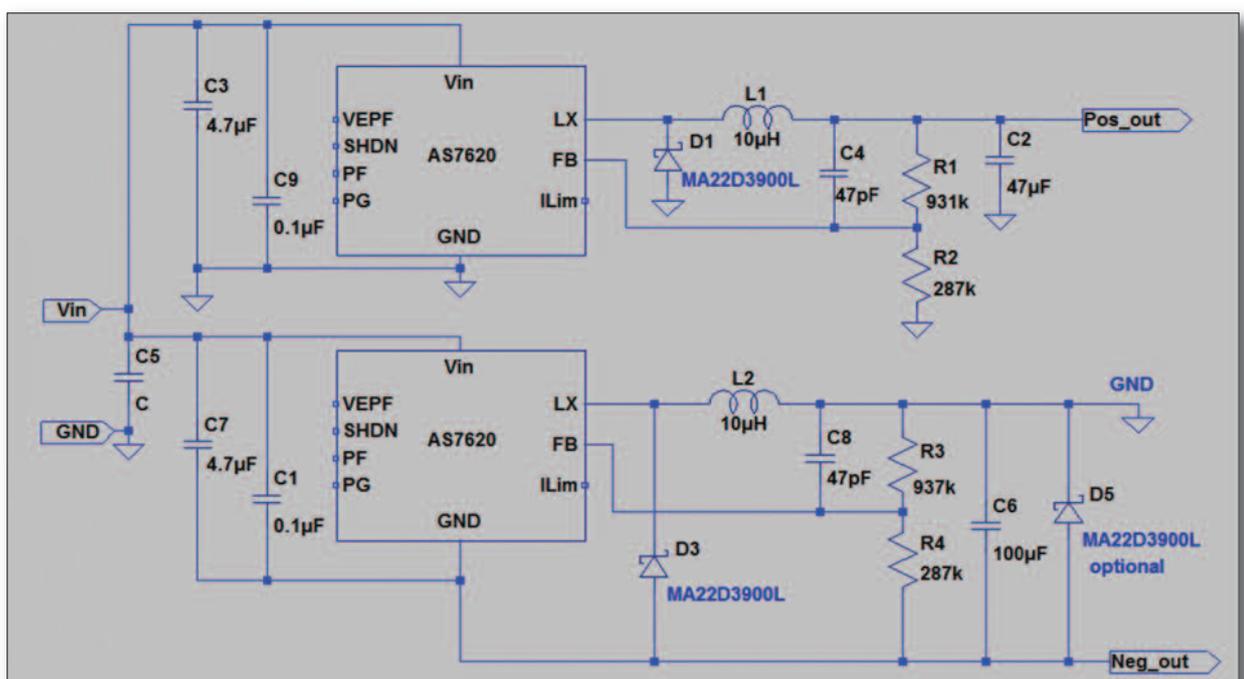


Figure 3: Two AS7620 buck regulators configured as a positive 5 V/500 mA regulator and a -5 V/250 mA regulator

So for noise-sensitive applications, additional filtering with a negative low drop-out regulator might be necessary.

Example of a working circuit

Figure 3 shows an example of a tested circuit for providing positive and negative 5 V output rails from a 12-24V supply. The positive 5 V output could generate up to 500 mA, while the -5 V output could safely provide a 250 mA output current while maintaining high efficiency.

When voltage is first applied to this circuit, the negative V_{out} rail will momentarily start to rise by a few hundred mV in the first 10 μ s or so, due to the action of the input capacitor. The magnitude of the positive rise on the negative rail will be a function of the size of the input capacitor; an optional Schottky diode across the output (D5 in Figure 3) can be added to clamp this voltage to below 300 mV. The output of this circuit is shown in Figures 4 and 5.

Design resources for implementing an inverting buck regulator circuit using the AS7620, including a datasheet with guidance on best layout practice, and information about a useful evaluation board, can be found at austriamicrosystem's website.

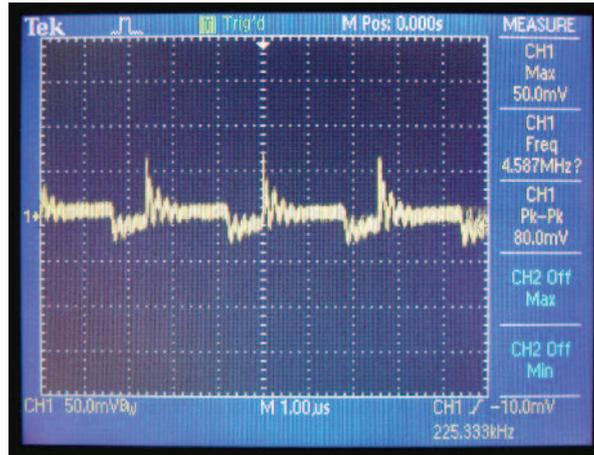


Figure 4: Steady state output voltage with 80 mVpp ripple


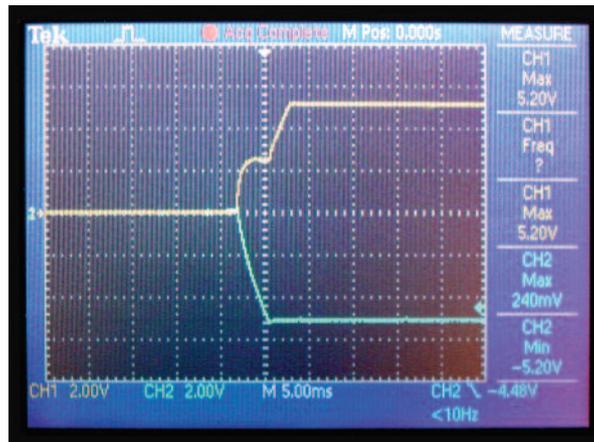


Figure 5: Start-up waveform for the +5 V and -5 V rails

www.electronicon.com

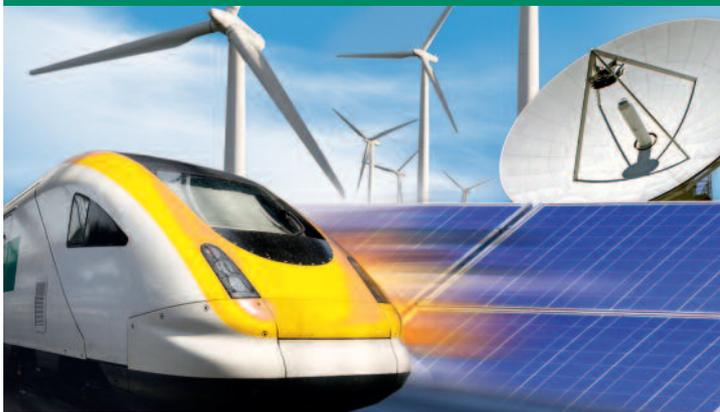

PK16™ High Density DC Filter Capacitors

The PK16™ capacitor can be universally used for the assembly of low inductance DC buffer circuits and DC filters; with its high energy density it can replace banks of series-connected electrolytic capacitors as well as large film capacitors in rectangular cases.

Create your own superior technical solution within existing or reduced space parameters

- superior voltage and current strength
- dramatic increase in operational life
- drastic reduction in failure rates
- minimization of power dissipation losses
- substantial reduction in self-inductance and series resistance
- more exact manufacturing tolerances
- elimination of sharing resistors

ELECTRONICON Kondensatoren GmbH · Keplerstrasse 2 · Germany - 07549 Gera · Fon: +49 365 7346 100 · email: sales@electronicon.com · web: www.electronicon.com



THE IDEAL CHOICE FOR YOUR DC LINK

ELECTRONICON®
always in charge